

Setting the Output Current with Resistance

“Can I dim the output current of my 0-10V driver with a resistor or potentiometer?”

Technically, yes. The 0-10V dimming lines sustain approximately 10V with an open connection. Resistance can be added across the dimming leads to serve as a voltage divider, effectively lowering the output current. This connection is shown in Figure 1.

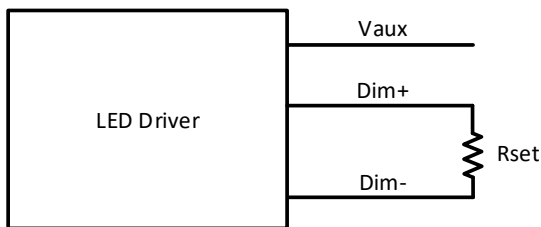


Figure 1: Wiring Diagram

Caution

It is not recommended to set the output current with resistance for everyday design and production. *Due to tolerances between individual drivers, the same resistance can result in different output currents on different drivers of the same model. Resistors and potentiometers also have tolerances, introducing even more deviation on the output.* For products needing a specific output current, we recommend our wide range of programmable drivers for best performance. The information in this note is intended to support situations where it is believed necessary to adjust the output current with resistance.

“What resistance do I need to set the output current?”

The resistance required will depend on the desired output current and the amount of current being sourced on Vdim (+).

The desired output current can be calculated as a percentage of the total output current. This percentage will correlate to a voltage on the 0-10V dimming leads (Vdim) as shown in Figure 2.

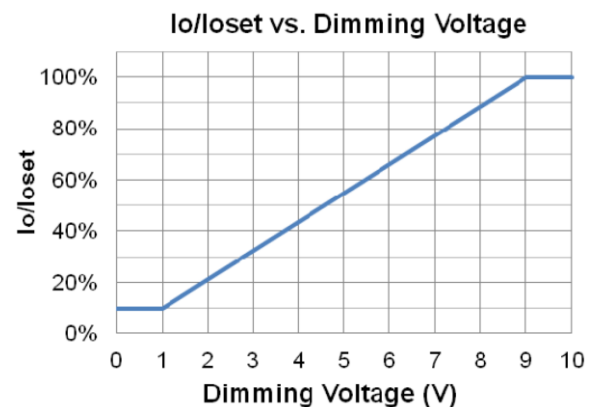


Figure 2: Output Current Percentage Dimming Voltage Correlation

The minimum output current percentage typically correlates with 1V and the maximum output current, or 100%, typically correlates with 9V. Though this curve can be referenced, Vdim can also be calculated using the following equations for drivers with a 10% minimum dim level and a 5% minimum dim level respectively:

$$V_{dim} = \frac{(8V)}{(90\%)} \times (Set\% - 10\%) + 1$$

$$V_{dim} = \frac{(8V)}{(95\%)} \times (Set\% - 5\%) + 1$$

The current sourced on the dimming leads (I_{source}) is specified under the “Dimming Specifications” of every datasheet, as shown below in Figure 3.

Source Current on Vdim (+) Pin	200 μ A	300 μ A	450 μ A
--------------------------------	-------------	-------------	-------------

Figure 3: Current Sourced on Vdim (+) Specification

Once the output current percentage and its correlated dimming voltage (V_{dim}) are defined, the resistance can be calculated using the following equation:

$$R_{set} = \frac{V_{dim}}{I_{source}}$$

If a design utilizes multiple drivers that all need to be set the same, a single resistance may be used. The current sourced on the dimming leads is additive, so the resistance will be divided by the total number of drivers’ (D_{total}) dimming leads paralleled together:

$$R_{set} = \frac{V_{dim}}{I_{source} \times D_{total}}$$

Quick Reference R_{set} Table

The **Appendix** includes a table that may be used as a quick reference to identify R_{set} .

Notice that the required resistance can vary dependent on the source current within the specified range. For best results, the source current is measured per individual driver and the correlated resistance is used. If the source current cannot be measured, please refer to the typical resistances that are highlighted in light blue.

Appendix Example

If using a single driver with a specified dimming source current of **200 μ A to 450 μ A** and a minimum dimming percentage of **5%**, the resistance required to set the output current to **70%** would be **21.58k Ω**

Note: please consider the **caution** outlined above.

Disclaimer

This note is for reference only. It is the responsibility of the customer to thoroughly analyze all aspects of the customers’ proposed application for the products. The customer is solely responsible for making the final selection of the product(s) to be used and to assure that all performance and safety requirements of the application are satisfied. Inventronics makes no representation or warranty as to the completeness or accuracy of the information contained herein. The products and specifications set forth in this document are subject to change without notice and Inventronics disclaims any and all liability for such changes.

Information presented in this note is subject to change without notice.

Appendix

Resistance to Set Output Current Percentage

Source Current on Vdim (+)	Minimum Diming Percentage	Output Current Percentage	1 Driver			2 Drivers			3 Drivers		
			Source Current Range (μA)			Source Current Range (μA)			Source Current Range (μA)		
			200	300	450	200	300	450	200	300	450
200μA to 450μA	10%	100%	45	30	20	22.5	15	10	15	10	6.67
		90%	40.56	27.04	18.02	20.28	13.52	9.01	13.52	9.01	6.01
		80%	36.11	24.07	16.05	18.06	12.04	8.02	12.04	8.02	5.35
		70%	31.67	21.11	14.07	15.83	10.56	7.04	10.56	7.04	4.69
		60%	27.22	18.15	12.1	13.61	9.07	6.05	9.07	6.05	4.03
		50%	22.78	15.19	10.12	11.39	7.59	5.06	7.59	5.06	3.37
		40%	18.33	12.22	8.15	9.17	6.11	4.07	6.11	4.07	2.72
		30%	13.89	9.26	6.17	6.94	4.63	3.09	4.63	3.09	2.06
		20%	9.44	6.3	4.2	4.72	3.15	2.1	3.15	2.1	1.4
		10%	5	3.33	2.22	2.5	1.67	1.11	1.67	1.11	0.74
0μA to 250μA	10%	100%	/	45	36	/	22.5	18	/	15	12
		90%	/	8.11	40.56	/	20.28	16.22	/	13.52	10.81
		80%	/	36.11	28.89	/	18.06	14.44	/	12.04	9.63
		70%	/	31.67	25.33	/	15.83	12.67	/	10.56	8.44
		60%	/	27.22	21.78	/	13.61	10.89	/	9.07	7.26
		50%	/	22.78	18.22	/	11.39	9.11	/	7.59	6.07
		40%	/	18.33	14.67	/	9.17	7.33	/	6.11	4.89
		30%	/	13.89	11.11	/	6.94	5.56	/	4.63	3.7
		20%	/	9.44	7.56	/	4.72	3.78	/	3.15	2.52
		10%	/	5	4	/	2.5	2	/	1.67	1.33
200μA to 450μA	5%	100%	45	30	20	22.5	15	10	15	10	6.67
		90%	40.79	27.19	18.13	20.39	13.6	9.06	13.6	9.06	6.04
		80%	36.58	24.39	16.26	18.29	12.19	8.13	12.19	8.13	5.42
		70%	32.37	21.58	14.39	16.18	10.79	7.19	10.79	7.19	4.8
		60%	28.16	18.77	12.51	14.08	9.39	6.26	9.39	6.26	4.17
		50%	23.95	15.96	10.64	11.97	7.98	5.32	7.98	5.32	3.55
		40%	19.74	13.16	8.77	9.87	6.58	4.39	6.58	4.39	2.92
		30%	15.53	10.35	6.9	7.76	5.18	3.45	5.18	3.45	2.3
		20%	11.32	7.54	5.03	5.66	3.77	2.51	3.77	2.51	1.68
		10%	7.11	4.74	3.16	3.55	2.37	1.58	2.37	1.58	1.05
		5%	5	3.33	2.22	2.5	1.67	1.11	1.67	1.11	0.74

*Resistance values are in kΩ.